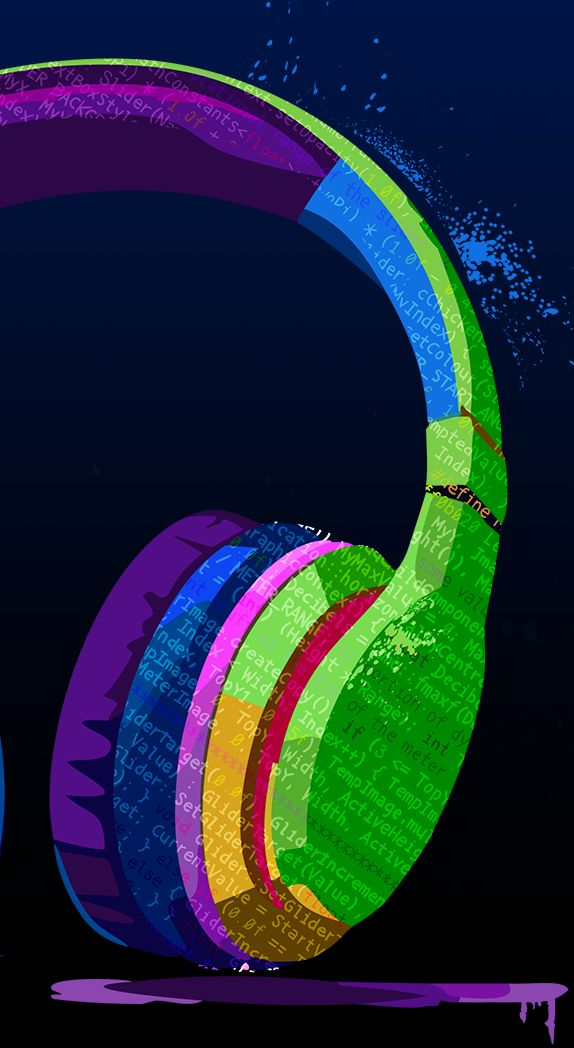




THE INTERSECTION OF ANALOG AND DIGITAL AUDIO PROCESSING

AN INTRODUCTORY GUIDE TO VIRTUAL ANALOG MODELLING


SOHYUN IM



About me

- **2021-2024:** BSc in Sound Engineering, University of West London
- **2024-present:** Master's student in Sound and Music Computing, Queen Mary University of London
- Amateur pianist
- ADC Diversity Scholarship recipient, 2022 and 2023.
- Giving my first talk at ADC24
- Participated in Dynamic Cast meetup

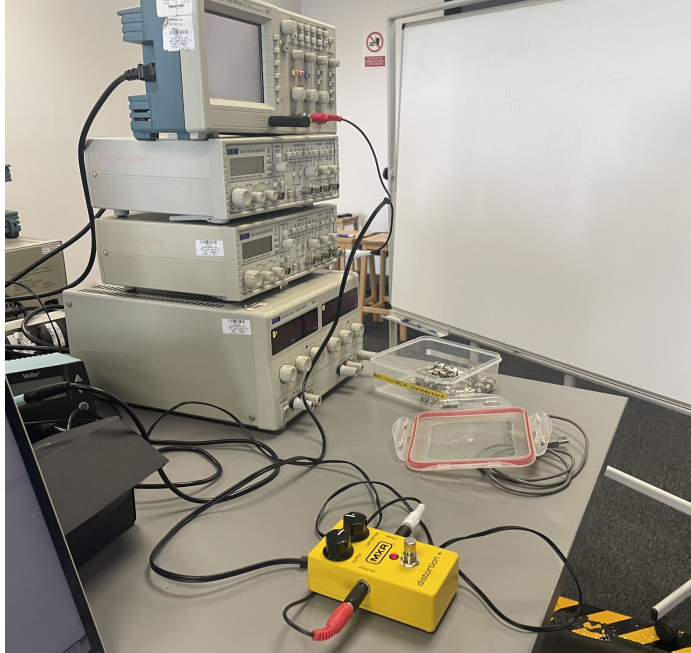A Little Background on the Project Behind This Talk



Electronics Lab at University of West London



Audio Developer Conference 2023

What I Aim to Share


- Simple yet concrete examples for newcomers to Virtual Analog Modelling
- Clarifying confusing terminology in the field
- Sharing the fun of understanding circuits

Repository



<https://github.com/Sohyun-Im/adctalk24>

What is Virtual Analog (VA) Modelling?

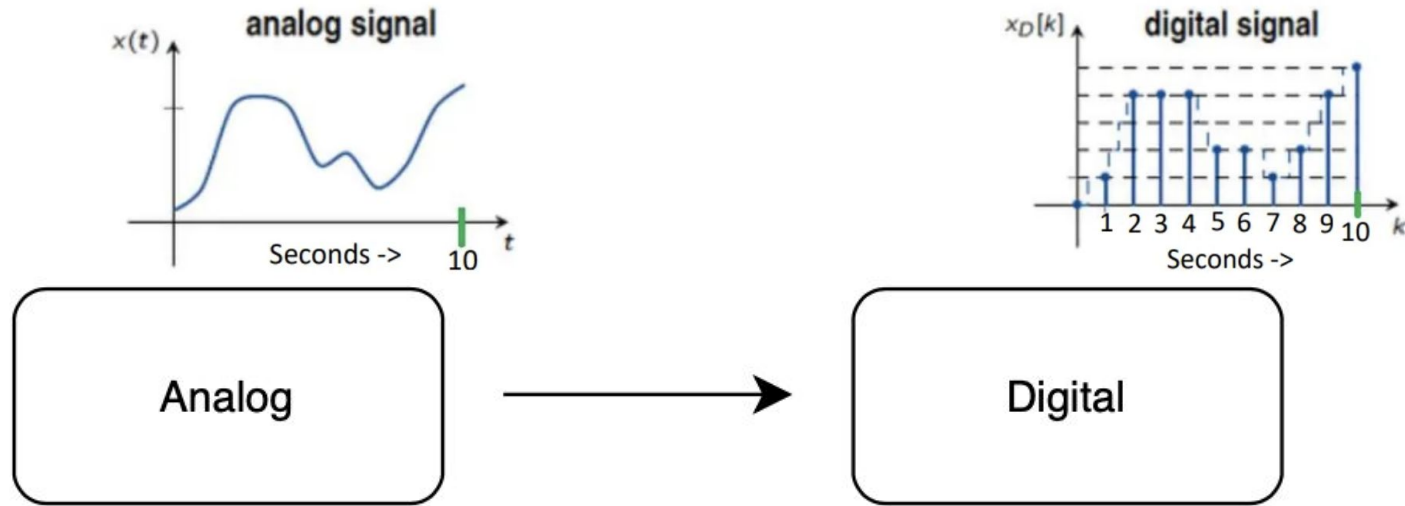


A system that processes continuous input/output signals that vary over time

A system processes discrete input/output signals at specific intervals over time.

What is Virtual Analog (VA) Modelling?



Analog

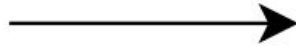


Digital



What is Virtual Analog (VA) Modelling?



Analog

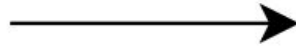

Digital

```
for n = 1:N
    % input-sample
    Vin = u(n,1);


    % transfer function to obtain the output-sample
    Vout = b0 * Vin + b1 * x1 + b2 * x2;

    % equations required for state updates
    Vx = (1/Gh)*Vout + ((R2*R4)/(Gb*Gh*R5))*x2;
    VR1 = (Vin-Vx*(R3*x1))/Gb;

    VR5 = (Vx-(R2*x2))/Gb;
    VR2 = (R2/R5)*VR5 + (R2*x2);

    % state update equations for C1 and C2
    x1 = (2/R1)*VR1 - x1;
    x2 = (2/R2)*VR2 - x2;

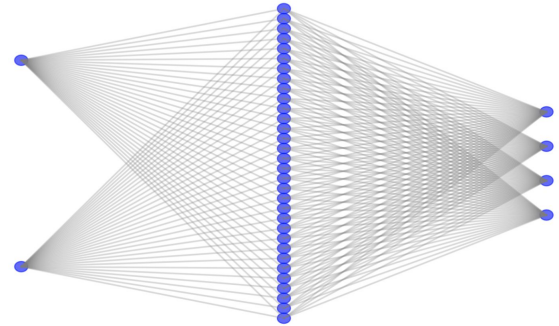    % y = output signal vector
    y(n,1) = Vout;
end
```



What is Virtual Analog (VA) Modelling?



```
for n = 1:N
    % input-sample
    Vin = u(n,1);

    % transfer function to obtain the output-sample
    Vout = b0 * Vin + b1 * x1 + b2 * x2;

    % equations required for state updates equations
    Vx = (1/Gh)*Vout + ((R2*R4)/(Gb*Gh*R5))*x2;
    VR1 = (Vin-Vx*(R3*x1))/Gb;


    VR5 = (Vx-(R2*x2))/Gb;
    VR2 = (R2/R5)*VR5 + (R2*x2);

    % state update equations for C1 and C2
    x1 = (2/R1)*VR1 - x1;
    x2 = (2/R2)*VR2 - x2;

    % y = output signal vector
    y(n,1) = Vout;
end
```



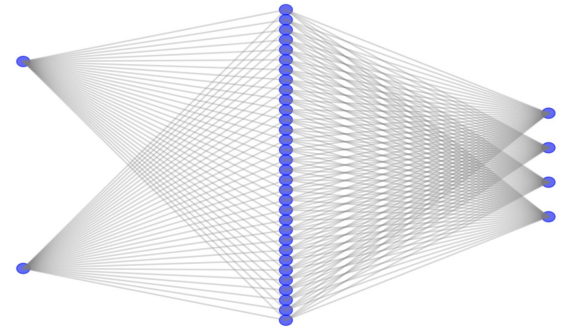Creating a **digital signal processor** that **mimics** the **electrical behaviour** of a **reference circuit**



VA Modelling vs Physical Modelling

Physical modelling

“... emulates the behaviour of sound-producing objects in the real world.”

e.g. acoustic instruments: piano, strings, etc.



Modartt - Pianoteq

Introduction to the Task

VA modelling of the **MXR *Distortion+*** guitar pedal based on circuit analysis methods

- Circuit analysis methods for analysing individual component and the complete circuit.
- Modelling by sub-circuit
- Implementation of Digital Signal Processing (DSP) using Python in Google Colab.
- Listening test: Comparison between VA-modelled DSP and the real pedal.


How Does It Sound Like?



MXR Distortion+

- **1970s** MXR Innovations
- **1987** Acquired by Jim Dunlop
- Randy Rhoads (w/ Ozzy Osbourne)
“Crazy Train”, “Mr. Crowley” (1980)
- Jerry Garcia in Grateful Dead
“Shakedown Street” (1978)

Overview of the Schematics

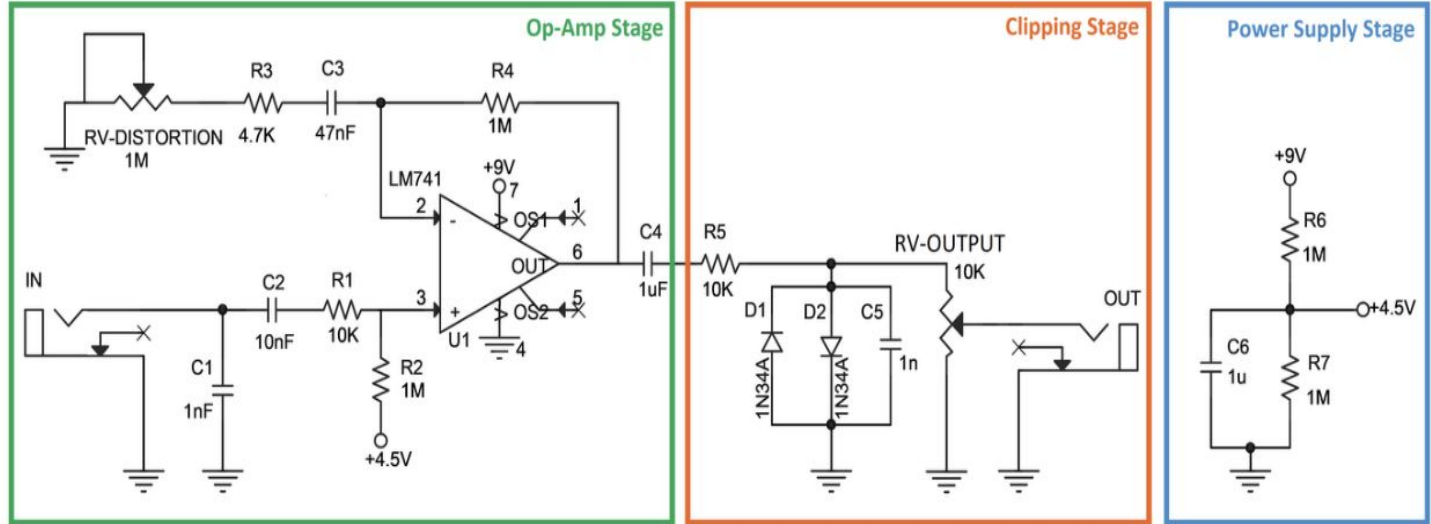

Some Prerequisite Knowledge (1) Voltage & Current

- Voltage (potential difference)
 - A pressure of electricity, which pushes electrons from a point of higher potential to a point of lower potential.
 - measured in volts (V)
- Current
 - The amount of electron flow in a circuit.
 - measured in amperes (A)

Some Prerequisite Knowledge (2) Components - Resistors



- Resistors limit the amount of current and divide voltage in a circuit, acting like a bottleneck
- Measured in Ohms(Ω)



Some Prerequisite Knowledge (2) Components - Capacitors



shutterstock.com · 1698844525

- Capacitors can store/release electrical energy.
- The current through a capacitor and the voltage across it keep changing.
- Measured in Farads (F)

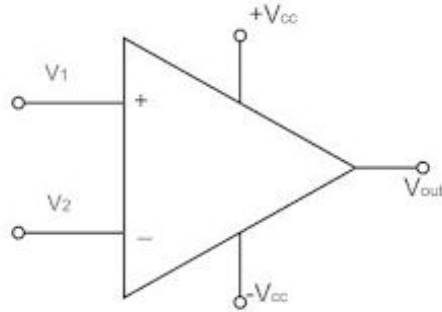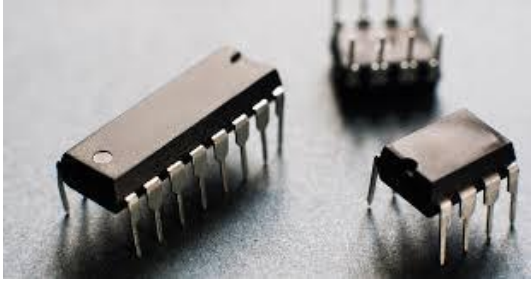Some Prerequisite Knowledge (2) Components - Operational Amplifiers (Op-amps)




Op-Amp Symbol

- High-gain voltage amplifier
- Two input terminals
 - inverting input
 - non-inverting input
- Key rules
 - If there's a feedback loop in a circuit, the voltages at the two input terminals are always equal.
 - No current flows into the two input terminals.

Some Prerequisite Knowledge (2) Components - Diodes




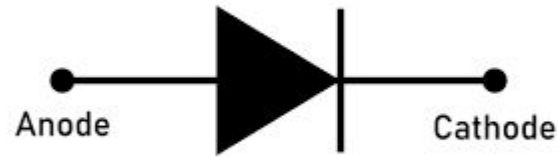- Current flows in one direction from the Anode to the Cathode, blocking reverse flow.




Some Prerequisite Knowledge (2) Components - Potentiometers (Variable Resistors)

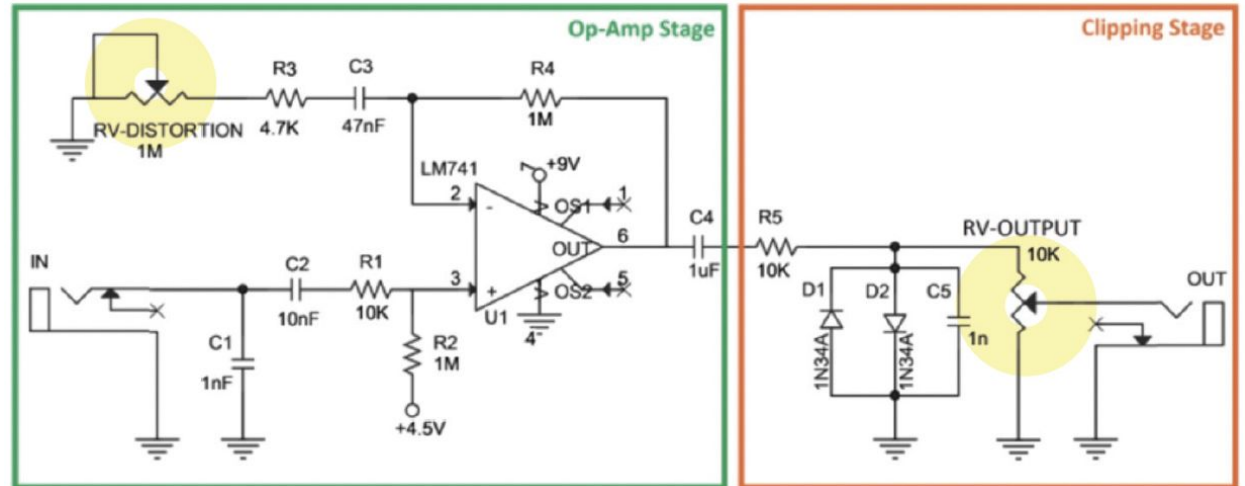- Potentiometers adjust resistance within a given range(Ω) to control voltage and current.




Some Prerequisite Knowledge (3) Kirchhoff's Law

kirchhoff's current law

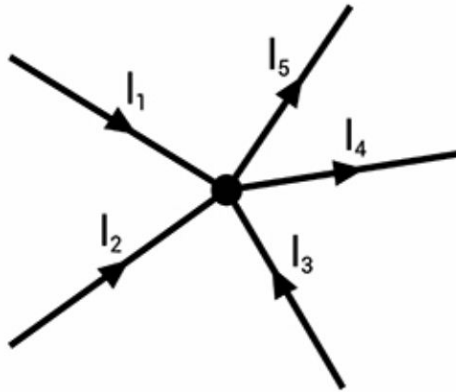

$$I_1 + I_2 + I_3 = I_4 + I_5$$

kirchhoff's voltage law

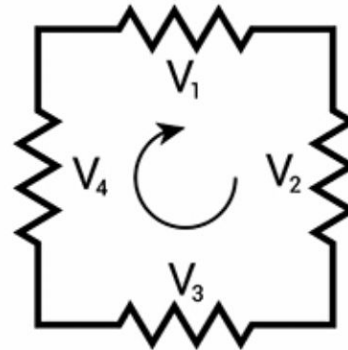

$$V_1 + V_2 + V_3 + V_4 = 0$$

Some Prerequisite Knowledge (4) Calculus

Differentiation and Derivative

- rate of change at a specific moment
- slope


Integration and Integral

- calculating the accumulated total.
- calculating the area under a function's curve

Circuit Analysis Methods

Circuit Analysis Method 1. Nodal Voltage Analysis (NVA)

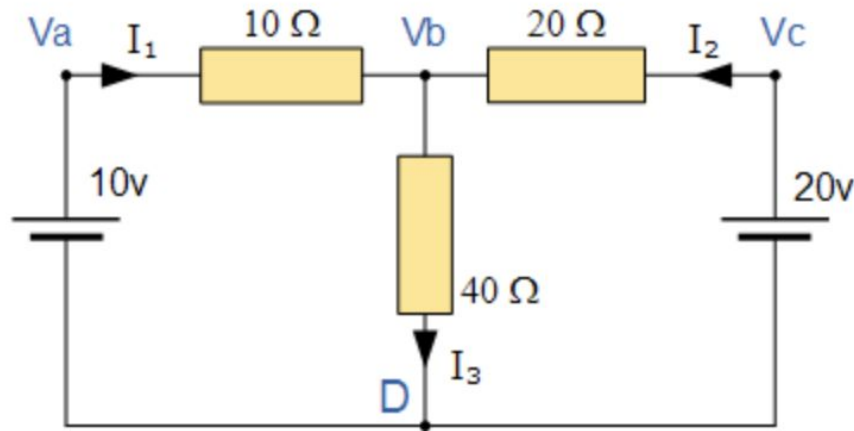- Label a node in the circuit with unknown voltage values
- Formulate equations using KCL or KVL for these nodes



$$\frac{(V_a - V_b)}{10} + \frac{(V_c - V_b)}{20} = \frac{V_b}{40}$$

$$V = I \times R$$

- **V** is the voltage (V)
- **I** is the current (A)
- **R** is the resistance (Ω)

Circuit Analysis Method 1. Nodal Voltage Analysis (NVA)

- Using NVA, we can further find out a mathematical expression that defines the relationship between input and output, known as the transfer function.
- This transfer function allows us to apply a discrete input to a system originally designed for continuous analog signals.

Circuit Analysis Method 2: Ohm's Law

- Ohm's Law expresses the relationship between voltage, current, and resistance in a circuit

$$V = I \times R$$

- V is the voltage (V)
- I is the current (A)
- R is the resistance (Ω)

Circuit Analysis Method 3: What about Capacitors?

- Finding the voltage across and the current through a capacitor is not as simple as with a resistor
- because a capacitor is dynamic component with time-varying voltage and current


3.1 Capacitance and current

The voltage across and the current through the capacitor over time



$$V_c = \frac{1}{C} \int I_c dt, \quad I_c = C \frac{dV_c}{dt}$$

(1) (2)

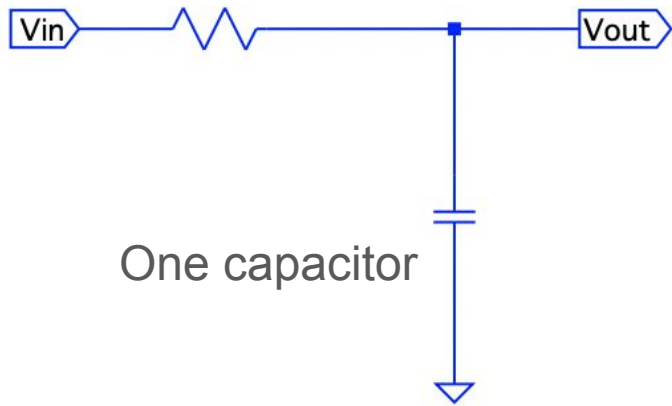3.2 Discrete Kirchhoff (DK) Substitution on Capacitors




One capacitor

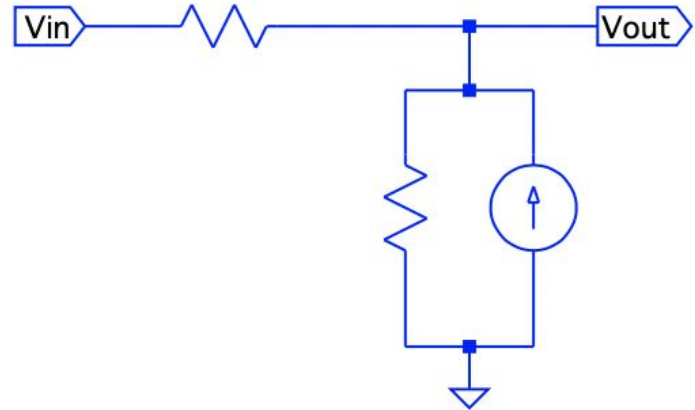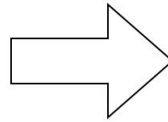

One resistor and one reversed current source in a parallel configuration

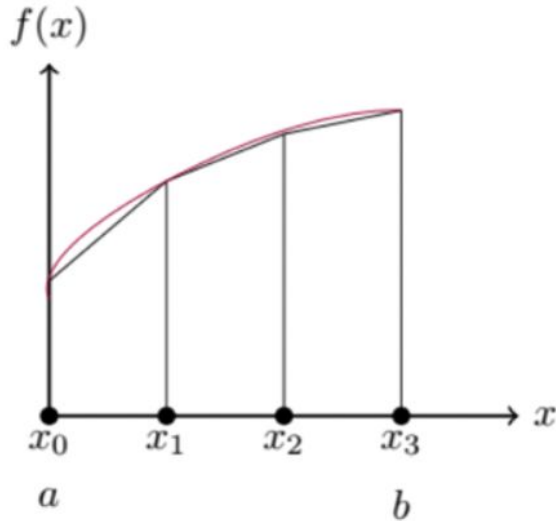3.3.1 The principles behind the DK substitution for capacitors



With respect to the discrete time point x_2 :


- The voltage across the capacitor is the area under the function's curve up to the x_2 .
- The current flowing through the capacitor is the rate of change of voltage multiplied by the capacitance.

$$(1) \quad V_c = \frac{1}{C} \int I_c dt, \quad (2) \quad I_c = C \frac{dV_c}{dt}$$

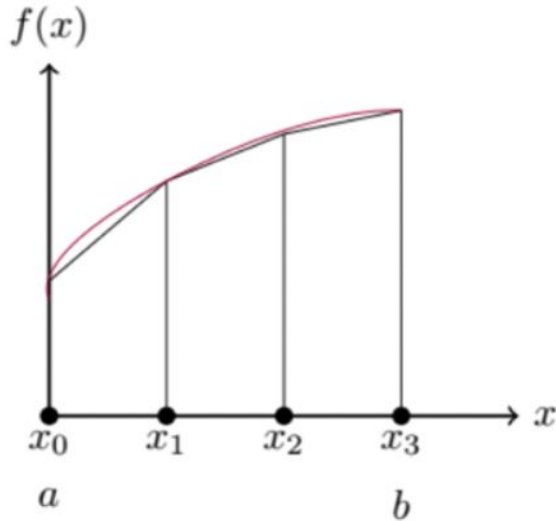3.3.2 The principles behind the dk substitution for capacitors

$$(1) \quad \int f(x_3)dt - \int f(x_2)dt = \left(\frac{f(x_2) + f(x_3)}{2} \right) \cdot T_s$$

Equation (1) represents the current flowing through the capacitor at the discrete time point x_2 as the difference between the accumulated voltage up to x_3 and that up to x_2 .



$$(2) \quad V[n] - V[n-1] = \frac{i[n] + i[n-1]}{2} \cdot T_s \cdot \frac{1}{C}$$

Equation (2) substitutes (1) into the discrete-time voltage change equation, reformulating it for the discrete signals n and $n-1$.

3.3.3 The principles behind the dk substitution for capacitors


$$(1) \quad V[n] - V[n-1] = \frac{i[n] + i[n-1]}{2} \cdot T_s \cdot \frac{1}{C}$$

$$(2) \quad i[n] = \frac{2C}{T_s} \cdot V[n] - \frac{2C}{T_s} \cdot V[n-1] - i[n-1]$$

$$(2.1) \quad X[n-1] = \frac{2C}{T_s} \cdot V[n-1] + i[n-1]$$


state value
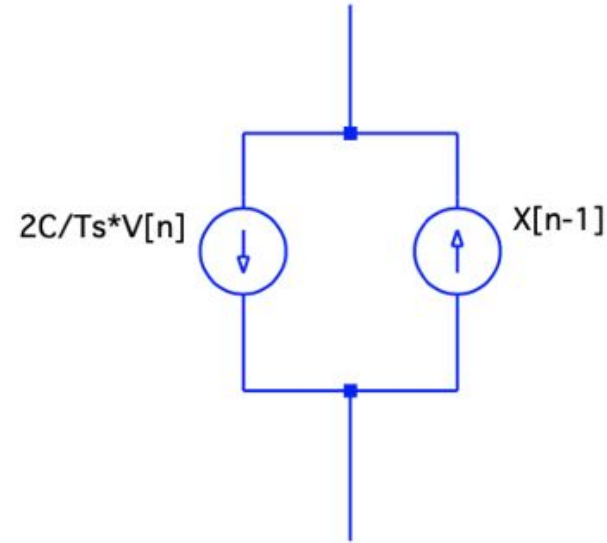
$$(3) \quad i[n] = \frac{2C}{T_s} \cdot V[n] - X[n-1]$$




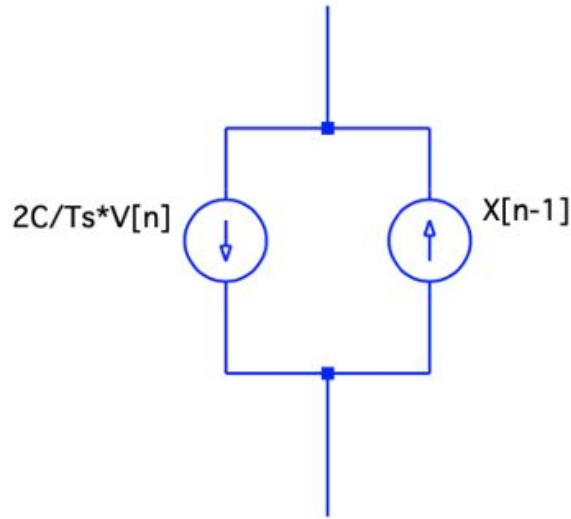3.3.4 The principles behind the dk substitution for capacitors

$$(1) \quad i[n] = \frac{2C}{T_s} \cdot V[n] - X[n-1]$$



(a)

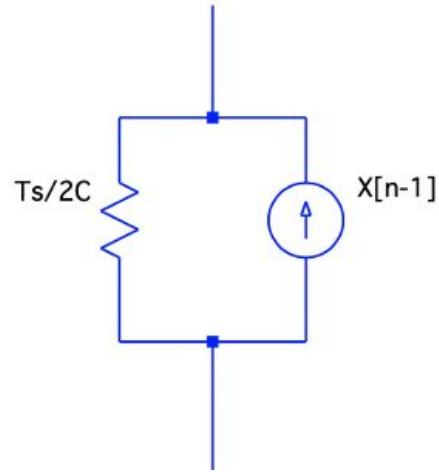


(b)

$$(2) \quad i = V[n] \cdot \frac{2C}{T_s}$$

$$(3) \quad \frac{1}{R} = \frac{2C}{T_s}$$

$$(4) \quad R = \frac{T_s}{2C}$$

3.4 state update equation

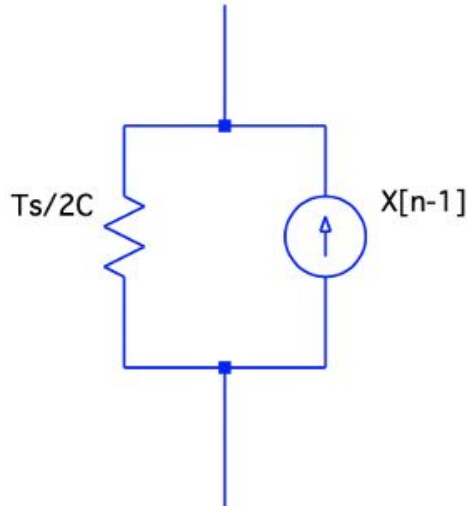

$$(1) \quad X[n-1] = \frac{2C}{T_s} \cdot V[n-1] + i[n-1]$$

$$(2) \quad X[n] = \frac{2C}{T_s} \cdot V[n] + i[n]$$

$$(3) \quad i[n] = \frac{1}{R} \cdot V[n] - X[n-1]$$


$$(4) \quad \therefore X[n] = \frac{2}{R} \cdot V[n] - X[n-1]$$

Method 3 Takeaways: Circuit Analysis with Capacitors

$$(1) \quad I_c = C \frac{dV_c}{dt} \quad \Rightarrow \quad i[n] = \frac{2C}{T_s} \cdot V[n] - X[n-1]$$

over time t

by discrete sample $[n]$

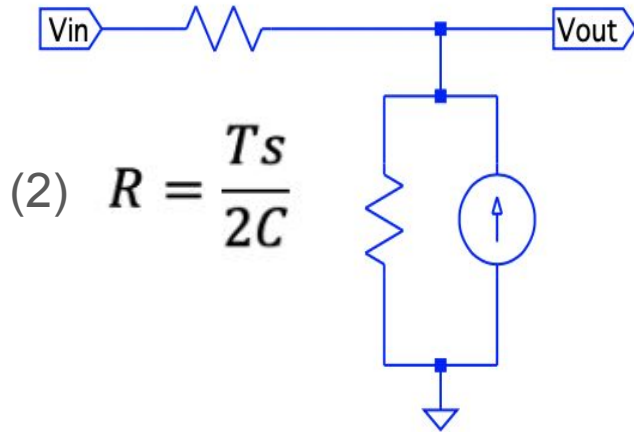

(3) State value


$$X[n-1] = \frac{2C}{T_s} \cdot V[n-1] + i[n-1]$$

(4) State-update equation

$$X[n] = \frac{2}{R} \cdot V[n] - X[n-1]$$


Method 4. About Diodes

- Back-to-back configuration: One diode conducts current when the signal flows in the positive direction, while the other diode conducts when the signal flows in the negative direction.
- Clipping voltage (0.7V): When the signal is below 0.7V, it passes through unaffected. However, when the signal exceeds 0.7V, current flows through the diode, limiting the signal at the 0.7V threshold and creating a clipping effect.

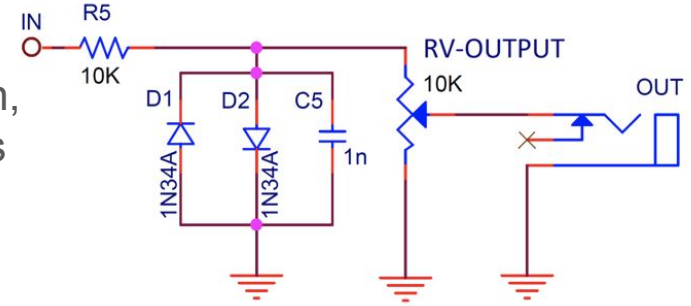

This results in **a distorted sound** in the pedal, where the fundamental pitch is preserved while additional harmonics are introduced, giving a richer and more aggressive tone.

Method 4.1 Shockley Diode Equations

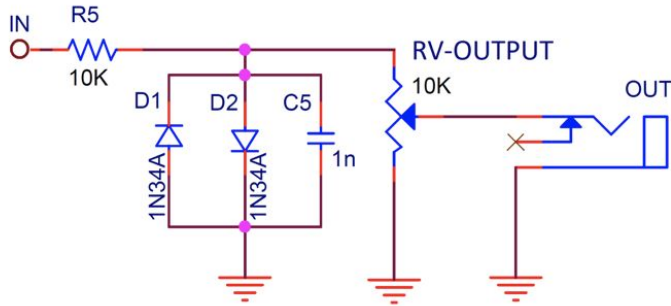

$$(1) \quad i_d = I_s * [e^{\left(\frac{V_d}{V_T \cdot \eta}\right)} - 1]$$

$$(2) \quad i_{d_pair} = 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{\eta \cdot V_T}\right)$$


Germanium diode params

Is = 10e-6 # saturation current

Vt = 0.026 # thermal voltage


eta = 2 # emission coefficient

Method 4.2 Newton-Raphson Method

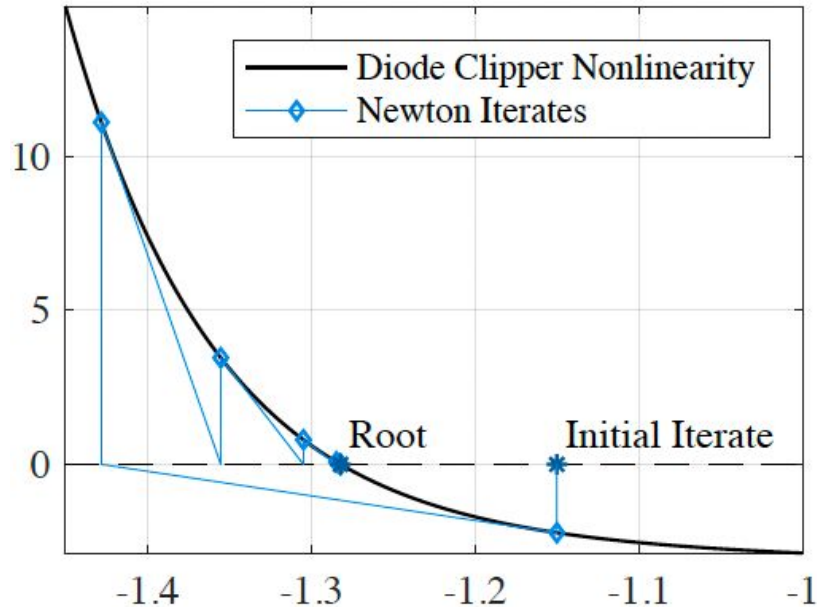

- To solve for V_d , the equation cannot be directly solved, because V_d is inside the $\sinh()$.
- To address this, the equation is rearranged so that all terms are on one side, and call this function $f(V_d)$.
- The goal is to find the value of V_d that makes this function $f(V_d) = 0$.
- Newton Raphson method starts with arbitrary point as a initial guess.
- Then the slope $f'(V_d)$ of the function at the initial point is calculated.
- Check where this slope intersects the x-axis,
- Check the function $f(V_d)$'s value. If it's not 0, repeat this process.

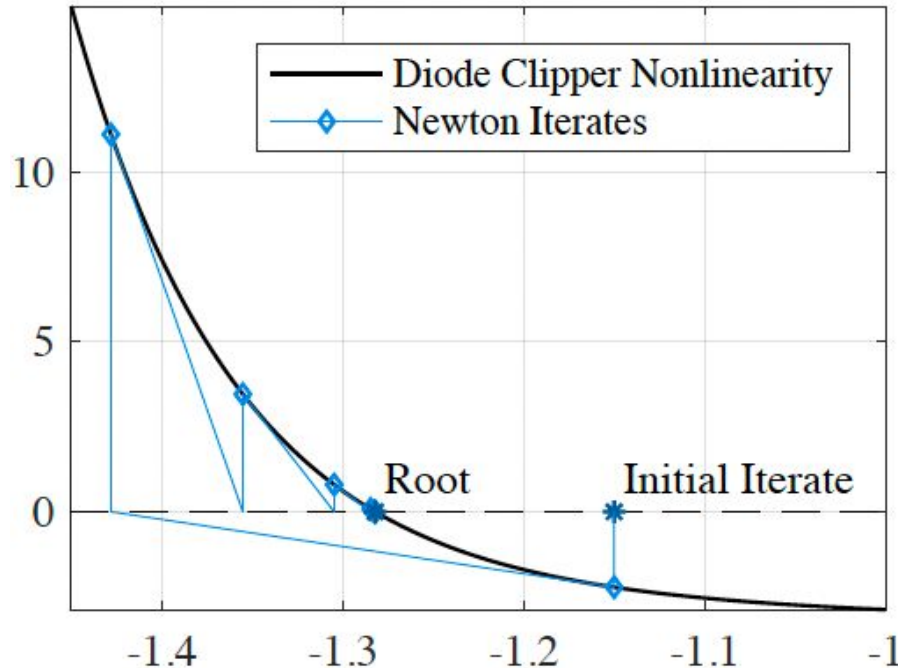Method 4.2 Newton-Raphson State Update Equation




$$f'(x_0) = \frac{f(x_0)}{x_0 - x_1} \quad (1)$$

$$x_1 = x_0 - \frac{f(x_0)}{f'(x_0)} \quad (2)$$


'x0' is the initial guess to find a root of the function, 'x1' is the second guess

Op-amp stage modelling

DK Substituted Circuit of Op-amp Stage

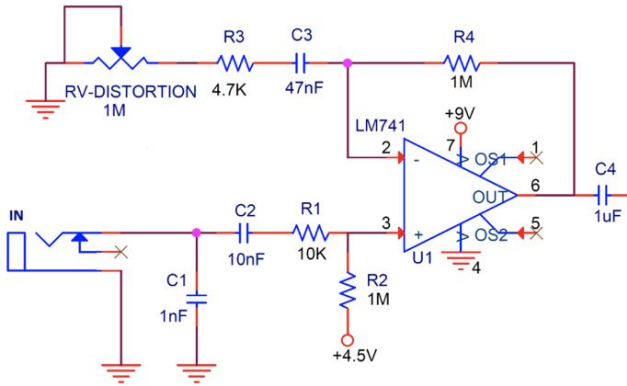

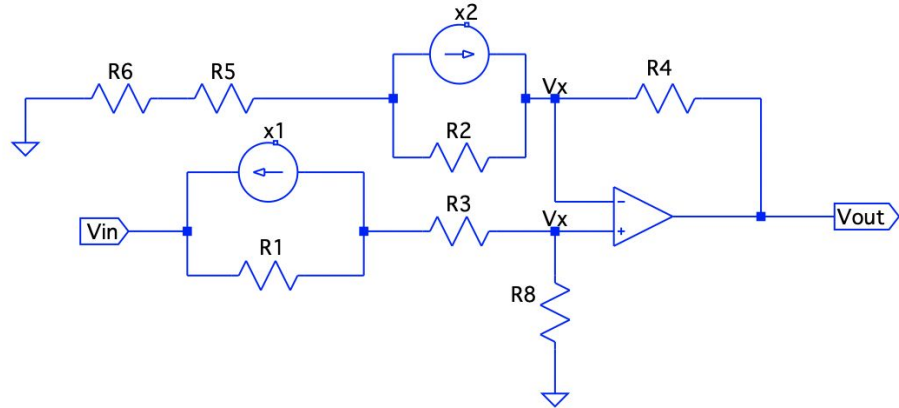
C1 and C4 are removed because those didn't affect the signal




- Components are re-labeled
- R6 is Distortion potentiometer (knob)

What We Aim to Find?

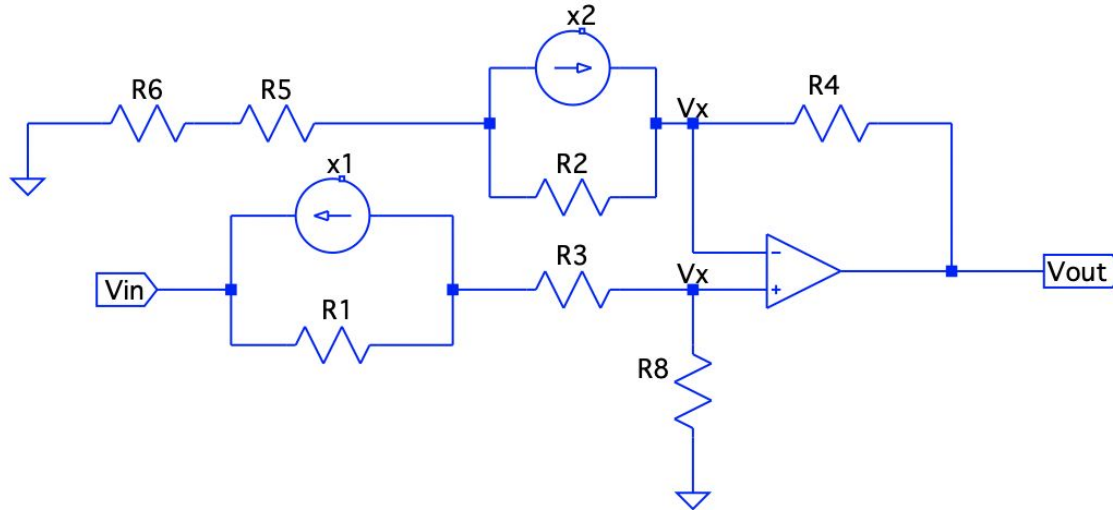- Set up two equations for V_x , then eliminate V_x .
- Derive the transfer function that represents the relationship between V_{in} and V_{out} .



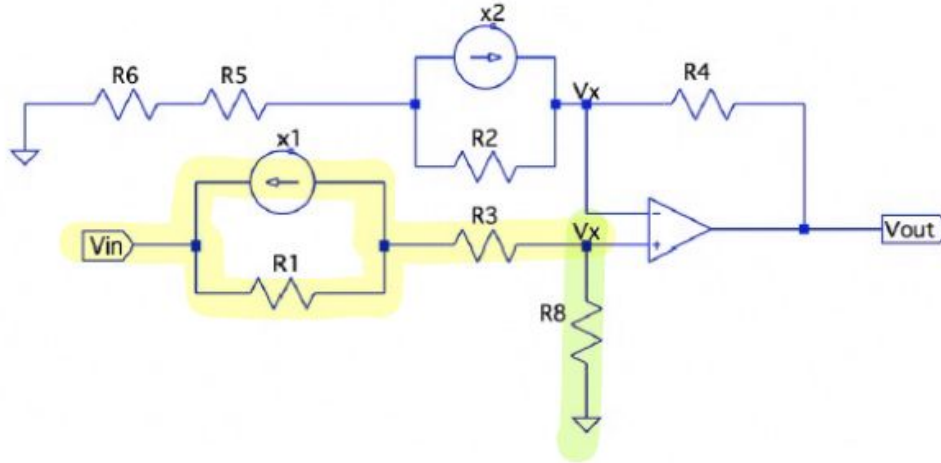
Process (1) Two branches of the input section



At the non-inverting input node V_x , using KCL, the following equation is derived based on the fact that the current flowing into V_x from V_{in} is equal to the current flowing out of V_x through $R8$

$$V_x = \frac{1}{G_a \cdot R1 \cdot G_x} \cdot V_{in} - \left(1 - \frac{R3}{G_a \cdot R1}\right) \left(\frac{x1}{G_x}\right)$$

Process (2) Potentiometer section

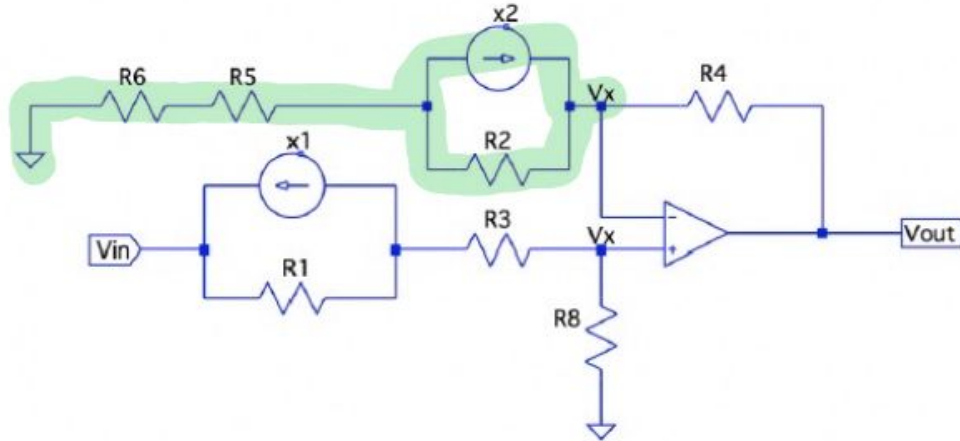


The current i_c , exiting the node V_x , is calculated using the fact that the current is the same throughout the segment, along with the equations for the current flowing through the resistor and capacitor.

$$i_c = \frac{V_x - R2 \cdot x2}{G_b \cdot Rn}$$

$$Rn = R5 + R6$$

Process (3) Feedback loop section

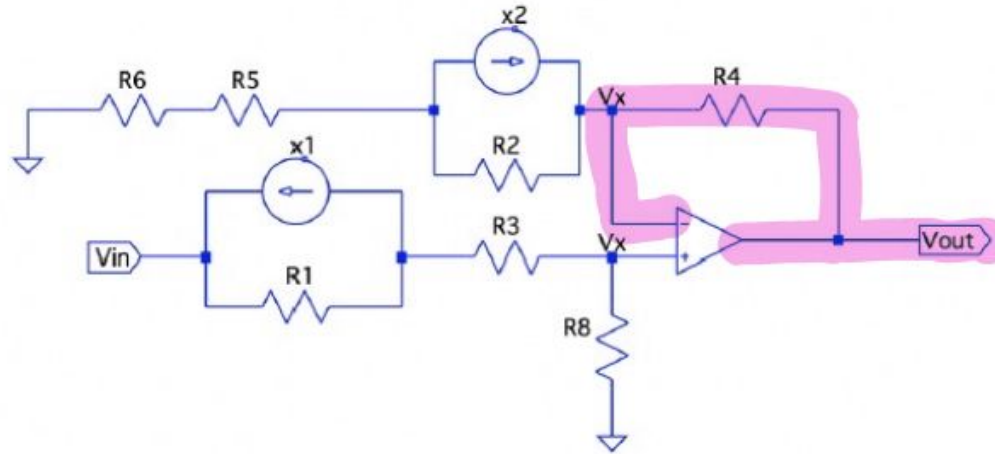

Using KCL wrt the node V_x with the obtained current value from the previous process, find the equation for V_x expressed with V_{out} and the component values.

$$V_x = \frac{1}{G_h} \cdot V_{out} + \frac{R_2 \cdot R_4}{G_b \cdot R_n \cdot G_h} \cdot x_2$$

Process (4) Transfer function

- The two equations for V_x obtained in Process (1) and Process (3) are formed a simultaneous equation.
- After V_x is eliminated, the transfer function of the Op-amp stage is obtained by solving the remained equation for V_{out} .

$$V_{out} = \frac{G_h}{G_a \cdot R1 \cdot G_x} \cdot V_{in} + \left(\frac{R3}{G_a \cdot R1} - 1 \right) \left(\frac{G_h}{G_x} \right) \cdot x1 + \left(\frac{-R2 \cdot R4}{G_b \cdot Rn} \right) \cdot x2$$

Process (5) State-update equation



When the $n+1$ th discrete signal is introduced, the state values for C1 and C2, will be updated through the state-update equations (1), (2).

$$(1) \quad x_1[n + 1] = \frac{2}{R_1} \cdot V_{R1} - x_1[n]$$


$$(2) \quad x_2[n + 1] = \frac{2}{R_2} \cdot V_{R2} - x_2[n]$$

Clipping stage modelling

DK Substitution of Clipping Stage

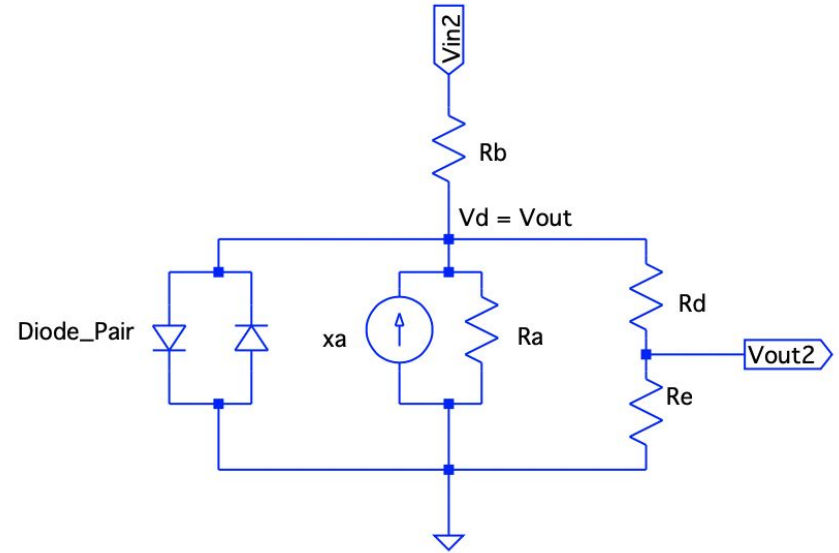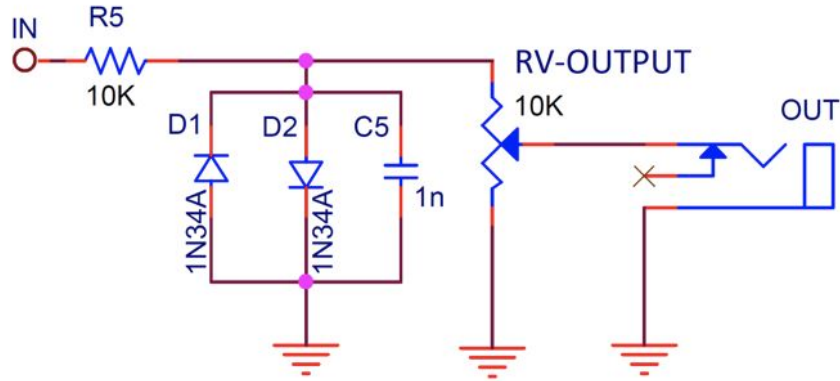

DK Substitution of Clipping Stage

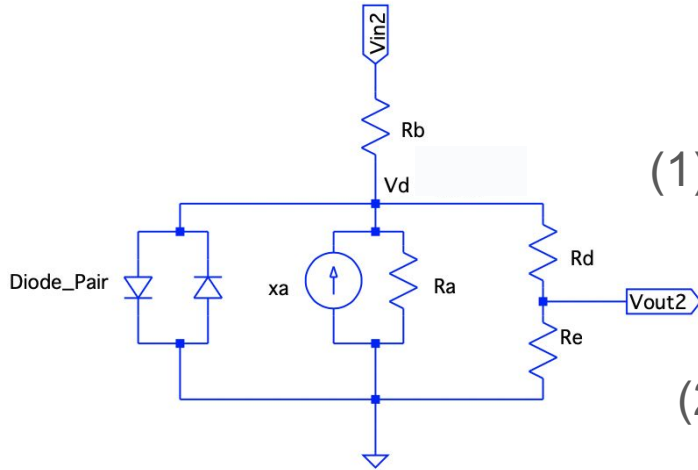

First, NVA for the node 'Vd' using KCL...

$$(1) \quad \frac{V_{in2} - V_d}{R_b} = 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{\eta \cdot V_T}\right) + \frac{V_d}{R_a} - x_a + \frac{V_d - V_{out2}}{R_d}$$

Second, move all terms of the equation (1) to one side and express it as a function $f(V_d)$ in terms of V_d .

$$(2) \quad f(V_d) = \frac{V_d}{R_b} - \frac{V_{in2}}{R_b} + 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{\eta \cdot V_T}\right) + \frac{V_d}{R_a} - x_a + \frac{V_d}{R_d} - \frac{V_{out2}}{R_d}$$


Third, calculate the derivative of the function $f(V_d)$ to determine the next guess for the Newton-Raphson iteration

$$(3) \quad f'(V_d) = \frac{1}{R_b} + \frac{1}{R_a} + \frac{1}{R_d} + \frac{2 \cdot I_s}{\eta \cdot V_T} \cdot \cosh\left(\frac{V_d}{\eta \cdot V_T}\right)$$

Newton-Raphson update equation

$$(4) \quad V_d = V_d - \frac{f(V_d)}{f'(V_d)}$$

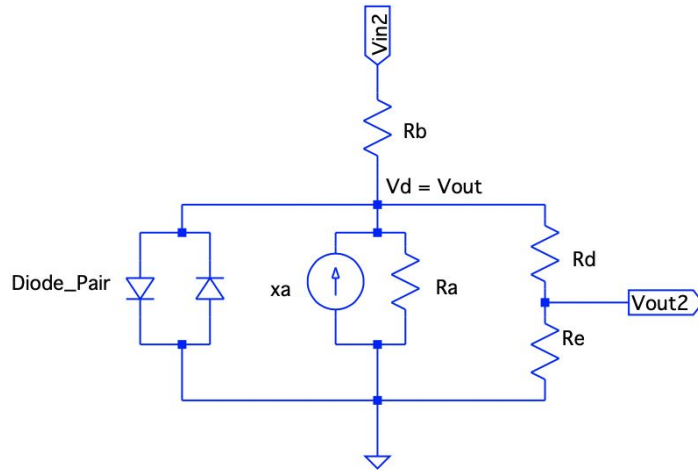Derive the Transfer Function for the Clipping Stage



By applying KCL,

$$\frac{V_d - V_{out2}}{R_d} = \frac{V_{out2}}{R_e}$$

By rearranging the equation wrt V_{out2} , the following transfer function for the clipping stage is derived.

$$V_{out2} = \frac{V_d}{R_d \cdot G_g}$$

DSP Implementation with Python (CoLab)

Takeaways

- Definition of Virtual Analog Modeling
- Various Circuit Analysis Methods for Discretizing Systems
 - Nodal Voltage Analysis
 - Ohm's Law for Resistors
 - DK Substitution for Capacitors
 - Shockley Diode Equation and Newton-Raphson Method for Diodes
- DSP Implementation with Python
- Listening Test

Q&A